

# Contents

Preface	vii
1. Introduction	1
1.1 What Is an NMR Probe . . . . .	1
1.1.1 The basic pulsed NMR experiment. . . . .	5
1.1.2 The head probe on a theoretical point of view. . . . .	9
1.1.2.1 The principle of reciprocity and the calculation of the induced emf . . . . .	9
1.1.2.2 Losses . . . . .	12
1.1.2.3 The ultimate sensitivity . . . . .	14
1.2 What Probes for a Specific NMR Experiment . . . . .	17
1.2.1 High resolution NMR in solution. . . . .	18
1.2.2 Solid state NMR. . . . .	19
1.2.3 Biomedical and Biophysical applications. . . . .	20
2. Relating the NMR Coil(s) to the Spectrometer	23
2.1 The NMR Spectrometer Major Parts . . . . .	25
2.1.1 General block scheme of an NMR spectrometer/imager . . . . .	25
2.1.2 Radio-frequency components. . . . .	25
2.1.2.1 Sources loads and transmission lines. . . . .	25
2.1.2.2 Transmitters. . . . .	29
2.1.2.3 Receivers. . . . .	32
2.1.2.4 Switching. . . . .	33
2.2 The NMR Probe Components . . . . .	35
2.2.1 Properties of RLC circuits. . . . .	35
2.2.1.1 Inductor. . . . .	35
2.2.1.2 Capacitor. . . . .	36
2.2.1.3 RLC circuits. . . . .	37
3. Matching the Probe Resonator to $50 \Omega$	47
3.1 Series Capacitive Matching . . . . .	48

3.2	Parallel Shunt Capacitive Coupling . . . . .	53
3.3	Inductive Matching . . . . .	56
3.3.1	Inductive matching with a single coupling loop. . . . .	60
3.3.2	Inductive matching with tuned coupling loop. . . . .	64
3.3.3	Inductive matching with fixed mutual and variable capacitor. . . . .	65
3.3.4	Repartition of current in the loops for inductive coupling. . . . .	72
3.4	Parallel Shunt Inductive Coupling . . . . .	73
3.5	Matching Using Transmission Lines . . . . .	76
3.6	Generalization of the NMR Probe Resonator Impedance Matching . . . . .	80
3.7	Broadband Matching. . . . .	88
3.8	Active Matching Network. . . . .	91
3.9	Balun Matching Network. . . . .	91
4.	Balancing the Probe Head . . . . .	93
4.1	Evidencing the Electric Losses Effect . . . . .	94
4.1.1	Experimental setup. . . . .	95
4.1.2	Frequency shifts. . . . .	98
4.1.3	Q factors. . . . .	100
4.2	Evidencing the Radiation Losses: the Antenna Effect. . . . .	101
4.3	The Common Mode Effects. . . . .	104
4.4	Optimizing the Sensitivity. . . . .	104
4.5	Symmetrical Capacitive Coupling Networks. . . . .	105
4.5.1	Splitting the matching capacitor. . . . .	105
4.5.2	A versatile capacitive balancing matching network. . . . .	108
4.5.3	A simple software to compute the matching components value . . . . .	119
4.6	LC-Balun Matching. . . . .	120
4.7	More Baluns. . . . .	123
4.8	Inductive Coupling Network. . . . .	128
5.	Quadrature Driving . . . . .	131
5.1	Low Frequency Transformers Circuit . . . . .	134
5.2	Quadrature Hybrid (Branch-Line Hybrid). . . . .	138
5.2.1	$\lambda/4$ transmission lines hybrid. . . . .	139
5.2.2	$\lambda/8$ transmission lines hybrid. . . . .	147
5.2.3	Lumped elements quadrature hybrids. . . . .	154
5.2.3.1	Quarter wave hybrid equivalent. . . . .	154
5.2.3.2	$\lambda/8$ hybrid equivalent. . . . .	158
5.2.4	Frequency response of the quad hybrids. . . . .	161
5.3	Ring Hybrid. . . . .	165
5.3.1	The $180^\circ$ rat-race hybrid. . . . .	166
5.3.2	Using the rat-race hybrid $180^\circ$ in quadrature NMR. . . . .	174
5.3.3	Lumped elements equivalent of the $180^\circ$ hybrid. . . . .	176

5.3.4	Frequency response of the 180° ring hybrid. . . . .	178
5.4	Other 90° Hybrids. . . . .	181
6.	Multiple Frequencies Tuning . . . . .	187
6.1	Shunting Methods. . . . .	190
6.1.1	Dual frequency switching circuits. . . . .	190
6.1.2	Practical double tuned circuits. . . . .	195
6.1.3	Multiple tuning of a single coil. . . . .	201
6.1.4	Symmetrizing the shunting configurations. . . . .	208
6.2	Multiple Poles Circuits. . . . .	213
6.3	Coupling Tank Circuits. . . . .	224
6.3.1	Coupled identical resonators. . . . .	227
6.3.2	Coupled resonators having the same resonance frequencies but different L/C ratio. . . . .	230
6.3.3	General case (different coupled resonators). . . . .	231
6.3.4	Fluxed coupled resonators. . . . .	233
6.3.5	Special case of a short circuited coil. . . . .	237
6.3.6	$\Pi$ – network configuration. . . . .	238
6.3.7	Summary of coupled resonators properties. . . . .	241
6.4	Efficiency for Multiple Tuned NMR Probe. . . . .	245
6.4.1	Efficiency for shunting methods. . . . .	245
6.4.2	Efficiency for multiple poles circuits. . . . .	249
6.4.3	Efficiency for coupled resonant circuits. . . . .	254
6.5	Is the Q Factor Representative for the Sensitivity? . . . . .	255
6.6	Connecting the Multiple Frequency Resonator to the Spectrometer . . . . .	258
7.	Magnetic Field Amplitude Estimation . . . . .	261
7.1	The Biot–Savart Approximation. . . . .	261
7.1.1	Magnetic field produced by straight wires. . . . .	263
7.1.2	Magnetic field produced by a loop. . . . .	266
7.2	Effective Field for NMR Experiments. . . . .	269
7.3	Estimation of the Current Distribution. . . . .	274
7.3.1	Limits and usefulness of the thin wire approximation. . . . .	274
7.3.2	Current distribution in the isolated flat strip. . . . .	276
7.3.3	Proximity effects. . . . .	285
7.3.3.1	Two coplanar strips. . . . .	285
7.3.3.2	Three or more strips. . . . .	287
7.3.3.3	Wire in proximity of a conductive plane. . . . .	288
7.3.4	Current density in round wires. . . . .	292
7.3.5	Concluding remarks. . . . .	294
7.4	Survey of Modern Electromagnetic Simulation Methods. . . . .	295

8. Homogeneous Resonators	301
8.1 Axial Resonators	303
8.1.1 Magnetic field amplitude	303
8.1.2 Approximations of the spherical uniform current density	307
8.1.2.1 Helmholtz coil	307
8.1.2.2 Four coils configuration	309
8.1.2.3 Guidelines for a practical design of Helmholtz probes and four coils probes	312
8.1.3 Solenoid types	314
8.1.3.1 The solenoid coil	314
8.1.3.2 The loop gap	319
8.1.3.3 Practical designs	324
8.2 Transverse Resonators	332
8.2.1 Magnetic field amplitude	332
8.2.2 The saddle shaped coil	335
8.2.2.1 The optimum geometry and RF magnetic field	335
8.2.2.2 A practical design	339
8.2.3 UHF saddle coil-like resonators	342
8.2.3.1 The Alderman–Grant coil, a version of the slotted cylinder	344
8.2.3.2 Coupling the Alderman–Grant resonator to the spectrometer, a practical design	348
8.2.3.3 The cosine, or Bolinger, coil	354
8.2.3.4 Double tuning the UHF saddle coil-like resonators, a practical design	364
8.2.3.5 Shielding the UHF saddle coil-like resonators	364
8.2.4 The birdcage resonator	371
8.2.4.1 RF field map of the birdcage design	372
8.2.4.2 Low-Pass, High-Pass, Band-Pass and Hybrid birdcage circuits	377
8.2.4.3 Tuning the birdcage resonator	387
8.2.4.4 Asymmetry effects	395
8.2.4.5 Relating the birdcage to the spectrometer	399
8.2.4.6 A practical design	401
8.2.4.7 Double tuning the birdcage resonator	414
8.2.5 The Litz coil	423
8.2.6 Transmission lines resonator	425
8.2.6.1 TEM resonators	425
8.2.6.2 Split transmission lines resonators	430
8.2.6.3 Ultra-fast recovery and ultra-broadband delay line probes	434

9. Heterogeneous Resonators	437
9.1 The Basic Surface Coil	437
9.1.1 The simple loop magnetic field distribution	439
9.1.1.1 "Ideal" case	439
9.1.1.2 Effect of inductive coupling	441
9.1.2 Practical design guidelines	447
9.1.2.1 How many turns?	447
9.1.2.2 Spiral windings	447
9.1.2.3 Arbitrary winding shapes	451
9.1.2.4 Wiring shape	453
9.1.2.5 Opened resonators	458
9.1.3 Surface coils for UHF	459
9.1.3.1 Segmented loop	459
9.1.3.2 The crossover-coil	461
9.1.3.3 Split ring resonator	462
9.1.3.4 Microstrip coils	464
9.1.4 Super conducting surface coils	466
9.1.5 Relating the coil to the spectrometer	468
9.2 Extending the Observed Volume (Multi-Rings Coils)	470
9.2.1 Coaxial rings	470
9.2.1.1 RF Field profiling	470
9.2.1.2 X-observed, proton decoupled system	473
9.2.2 Array coils	475
9.3 The Surface Coil as Receive-Only Probe	479
9.3.1 Passive decoupling	480
9.3.2 Active decoupling	488
10. Probe Evaluation and Debugging	493
10.1 Adjusting and Evaluating the Probe	493
10.1.1 Instrumentation	494
10.1.1.1 The pick-up coil	494
10.1.1.2 The "grid-dip"	494
10.1.1.3 Impedance bridge	495
10.1.1.4 Power divider, hybrid and directional coupler	498
10.1.1.5 Sweep generator, crystal detector and spectrum analyzer	500
10.1.1.6 Scalar and vector network analyzer	503
10.1.2 Evaluating the probe on the RF workbench	504
10.1.2.1 Matching the probe input impedance to $50\ \Omega$	504
10.1.2.2 Evaluation of Q factor	507
10.1.2.3 $B1/\sqrt{P}$ evaluation methods	510
10.1.3 Evaluating the probe connected to the NMR spectrometer	513

10.2 Useful Information. . . . .	516
10.2.1 Self and mutual inductance calculations. . . . .	516
10.2.1.1 Formulae. . . . .	516
10.2.1.2 Integration methods. . . . .	521
10.2.1.3 Evaluation of the complete elliptic integrals . . . . .	522
10.2.2 The solenoid . . . . .	523
10.2.3 Introduction to network theory. . . . .	527
10.2.3.1 Impedance and admittance matrices. . . . .	529
10.2.3.2 The transmission (ABCD) matrix. . . . .	532
10.2.3.3 The scattering matrix. . . . .	533
10.2.4 Transmission lines. . . . .	534
10.2.4.1 Electrical properties. . . . .	534
10.2.4.2 Transmission line designs. . . . .	538
10.2.4.3 Lumped elements replacement of lines. . . . .	541
Appendix A. Solving Impedance Matching. . . . .	545
Appendix B Current Distribution Calculation. . . . .	549
Appendix C Magnetic Field Distribution Estimation . . . . .	555
Appendix D A Simple Linear Network Analysis Program. . . . .	563
Bibliography. . . . .	573
<i>Index</i> . . . . .	593